
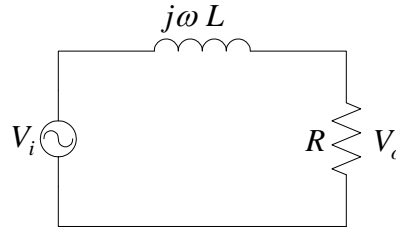

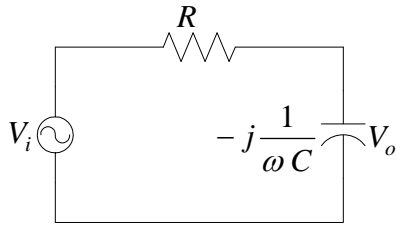
## Frequency selective circuits

**Low pass Filters** are used to pass low-frequency sine waves and attenuate high frequency sine waves. The *cutoff* frequency  $\omega_c$  is used to distinguish the passband ( $\omega_c < \omega$ ) from the stopband ( $\omega_c > \omega$ ). An elementary example of two passive lowpass filter is given below.



$$\frac{V_o}{V_i} = \frac{1}{1 + j\omega RC} \quad (1)$$

$$\frac{V_o}{V_i} = \frac{1}{1 + j\omega \frac{L}{R}}$$

$$\frac{|V_o|}{|V_i|} = \frac{1}{[1 + (\omega RC)^2]^{1/2}} \quad (2)$$

$$\frac{|V_o|}{|V_i|} = \frac{1}{\left[1 + \left(\omega \frac{L}{R}\right)^2\right]^{1/2}}$$

$$\theta = -\tan^{-1} \omega RC \quad (3)$$

$$\theta = -\tan^{-1} \omega \frac{L}{R}$$

At cutoff frequency Gain =  $1/\sqrt{2}$ . Substituting in (2) result in



$$\omega_c = \frac{1}{RC} \quad (4)$$

$$\omega_c = \frac{R}{L}$$



From (3), we see that the phase angle at cutoff frequency is  $-45^\circ$

The ratio  $\frac{V_o}{V_i}$  is shown by  $H(j\omega)$ , and is called the *frequency response transfer function*.

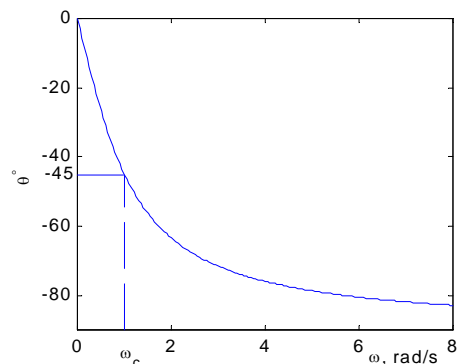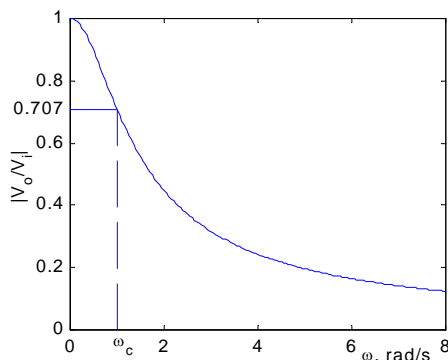The gain versus frequency, and the phase angle versus frequency known as the *frequency response* is as shown.



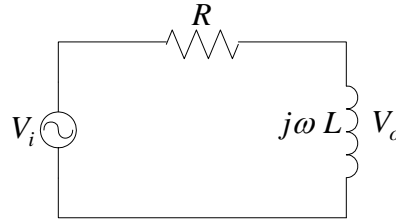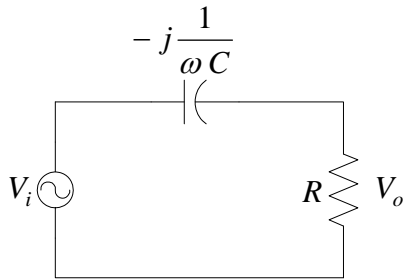**High pass Filters** are used to stop low-frequency sine waves and pass the high frequency sine waves. The *cutoff* frequency  $\omega_c$  is used to distinguish the stopband ( $\omega_c < \omega$ ) from the passband ( $\omega_c > \omega$ ). An elementary example of two passive highpass filter is given below.



$$\frac{V_o}{V_i} = \frac{\omega RC}{\omega RC - j1} \quad (5)$$

$$\frac{V_o}{V_i} = \frac{\omega \frac{L}{R}}{\omega \frac{L}{R} - j1}$$

$$\frac{|V_o|}{|V_i|} = \frac{\omega RC}{\left[ (\omega RC)^2 + 1 \right]^{1/2}} \quad (6)$$

$$\frac{|V_o|}{|V_i|} = \frac{\omega \frac{L}{R}}{\left[ \left( \omega \frac{L}{R} \right)^2 + 1 \right]^{1/2}}$$

$$\theta = \tan^{-1} \frac{1}{\omega RC} \quad (7)$$

$$\theta = \tan^{-1} \frac{R}{\omega L}$$



At cut off frequency Gain =  $1/\sqrt{2}$ . Substituting in (6) result in

$$\omega_c = \frac{1}{RC}$$

$$\omega_c = \frac{R}{L}$$


From (7), we see that the phase angle at cutoff frequency is  $45^\circ$

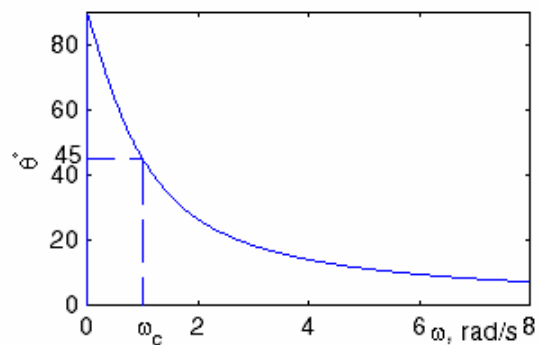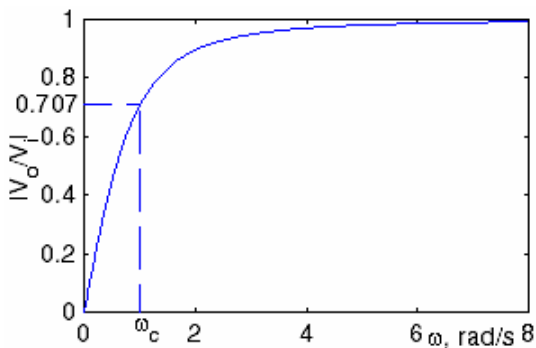The gain versus frequency, and the phase angle versus frequency known as the *frequency response* is as shown.



## Bandpass Filters

### (a) The Parallel RLC Resonance

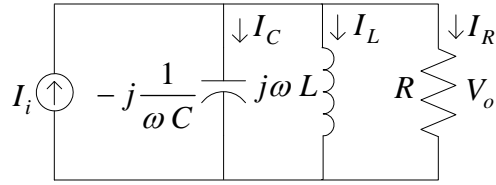


$$V_o = \frac{I_i}{\frac{1}{R} + j\left(\omega C - \frac{1}{\omega L}\right)}$$

A circuit is in resonance when the voltage and current at the input terminals are in phase.

The circuit admittance is  $Y = \frac{1}{R} + j\left(\omega C - \frac{1}{\omega L}\right)$ . At resonance  $Y$  is purely conductive and

$\omega C - \frac{1}{\omega L} = 0$ , thus  $\omega_o = \frac{1}{\sqrt{LC}}$ . The circuit admittance is minimum or the circuit

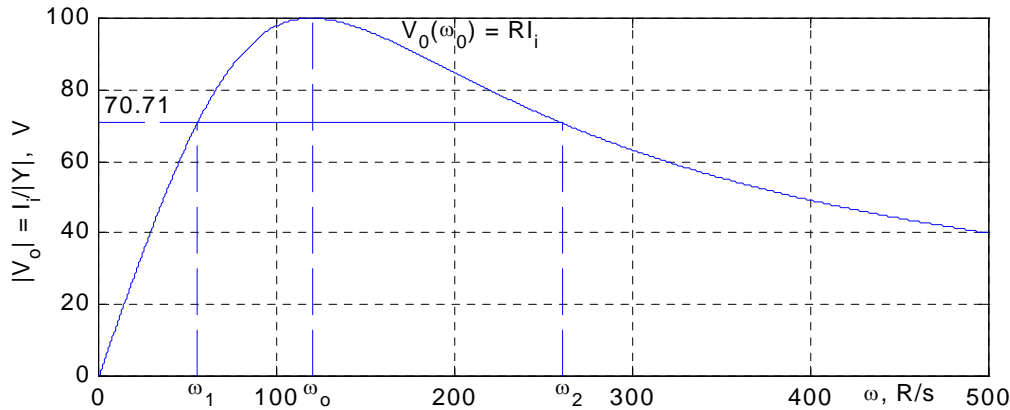impedance at resonance, given by  $Z(\omega_o) = R$ , is maximum. Thus, the output voltage at resonance is maximum and is given by  $V_o(\omega_o) = RI_i$



The frequencies  $\omega_1$  and  $\omega_2$  at which the output power drops to one half of its values at the resonant frequency are called the *half-power frequencies*. At these frequencies also known as *cutoff frequencies* or *corner frequencies*, the output voltage is

$|V_o(\omega_c)| = 0.707 |V_o(\omega_o)|$ . This circuit which passes all the frequencies within a band of

frequencies ( $\omega_1 < \omega < \omega_2$ ) is called a *bandpass filter*. This range of frequency is known as the circuit *bandwidth*.

$$\beta = \omega_2 - \omega_1$$

The half-power frequencies are obtained from

$$|V_o(\omega_c)| = \frac{I_i}{\left[ \left(\frac{1}{R}\right)^2 + \left(\omega C - \frac{1}{\omega L}\right)^2 \right]^{\frac{1}{2}}} = \frac{1}{\sqrt{2}} RI_i$$

Solving for  $\omega$  we obtain

$$\omega_1 = -\frac{1}{2RC} + \sqrt{\left(\frac{1}{2RC}\right)^2 + \frac{1}{LC}}, \text{ and } \omega_2 = \frac{1}{2RC} + \sqrt{\left(\frac{1}{2RC}\right)^2 + \frac{1}{LC}}$$

From the above, we obtain,  $\omega_2 - \omega_1 = \frac{1}{RC}$ , or the circuit bandwidth is

$$\beta = \frac{1}{RC}$$

The cutoff frequencies can be written in terms of  $\omega_0$  and  $\beta$  as follow:

$$\omega_1 = -\frac{\beta}{2} + \sqrt{\left(\frac{\beta}{2}\right)^2 + \omega_o^2}, \text{ and } \omega_2 = \frac{\beta}{2} + \sqrt{\left(\frac{\beta}{2}\right)^2 + \omega_o^2}$$

This shows that  $\omega_o$  is the geometric mean of  $\omega_1$  and  $\omega_2$ , i.e.,

$$\omega_o = \sqrt{\omega_1 \omega_2}$$

Notice that  $\beta$  is inversely proportional to  $R$ , i.e., smaller  $R$  results in a larger bandwidth.

The resonant frequency ( $\omega_o = \frac{1}{\sqrt{LC}}$ ) is a function of  $L$  and  $C$ . Therefore, by adjusting  $L$  and  $C$  a desired resonant frequency is obtained, whereas by adjusting  $R$ , the bandwidth and the height of the response curve is adjusted. The sharpness of the resonance is measured quantitatively by the *quality factor*  $Q$ . This is defined as the ratio of the resonant frequency to the bandwidth.


$$Q = \frac{\omega_o}{\beta}$$

Substituting for  $\beta = \frac{1}{RC}$  and  $\omega_o = \frac{1}{\sqrt{LC}}$  the quality factor can be expressed as

$$Q = \omega_o RC = \frac{R}{\omega_o L} = R \sqrt{\frac{C}{L}}$$


At resonance  $I_L$  and  $I_C$  are given by
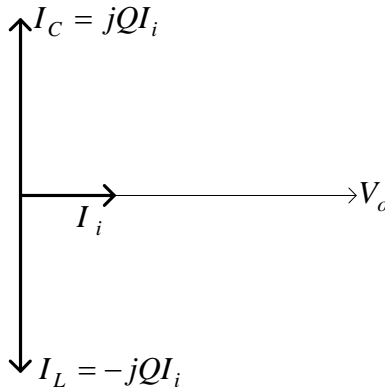
$$I_L = \frac{V_o}{j\omega_o L} = -j \frac{V_o}{R/Q} = -jQI_i \text{ and } I_C = j\omega_o CV_o = j \frac{Q}{R} V_o = jQI_i$$



As it can be seen at resonance depending on the  $Q$  factor,  $I_L$  and  $I_C$  can be many times the supply current (current amplification).

**(b) The Series RLC Resonance**

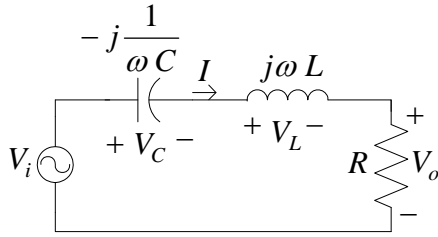


$$I = \frac{V_i}{R + j(\omega L - \frac{1}{\omega C})}$$

A circuit is in resonance when the voltage and current at the input terminals are in phase.

The circuit impedance is  $Z = R + j(\omega L - \frac{1}{\omega C})$ . At resonance  $Z$  is purely resistive and

$\omega L - \frac{1}{\omega C} = 0$ , thus  $\omega_o = \frac{1}{\sqrt{LC}}$ . The circuit impedance at resonance, given

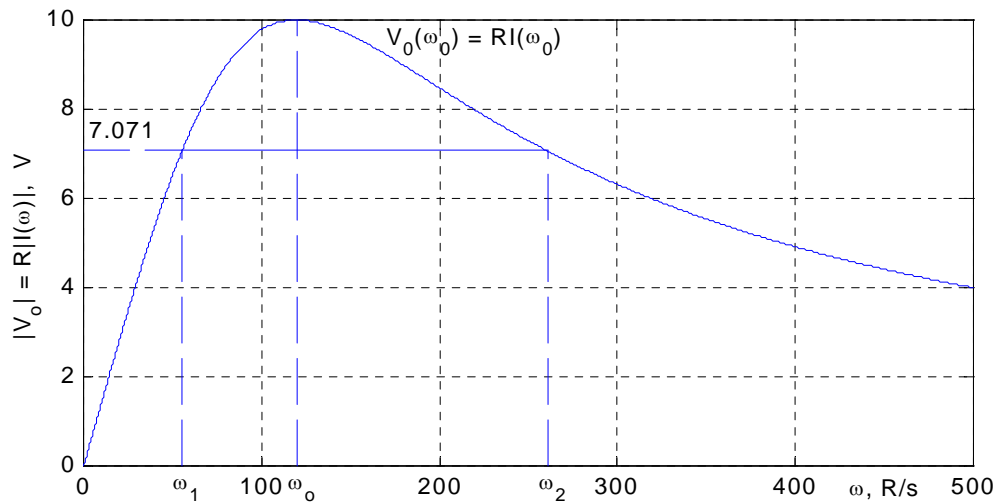by  $Z(\omega_o) = R$  is minimum, and the current is maximum. Thus, the output voltage at resonance is maximum and is given by  $V_o(\omega_o) = RI(\omega_o)$



The frequencies  $\omega_1$  and  $\omega_2$  at which the output power drops to one half of its values at the resonant frequency are called the *half-power frequencies*. At these frequencies also known as *cutoff frequencies* or *corner frequencies*, the output voltage is  $|V_o(\omega_c)| = 0.707 |V_o(\omega_o)|$ . This circuit which passes all the frequencies within a band of frequencies ( $\omega_1 < \omega < \omega_2$ ) is called a *bandpass filter*. This range of frequency is known as the circuit *bandwidth*.

$$\beta = \omega_2 - \omega_1$$

The half-power frequencies are obtained from

$$|V_o(\omega_c)| = R \frac{V_i}{\left[ (R)^2 + \left( \omega L - \frac{1}{\omega C} \right)^2 \right]^{\frac{1}{2}}} = \frac{1}{\sqrt{2}} V_i$$

Solving for  $\omega$  we obtain

$$\omega_1 = -\frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}}, \text{ and } \omega_2 = \frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}}$$

From the above, we obtain,  $\omega_2 - \omega_1 = \frac{R}{L}$ , or the circuit bandwidth is

$$\beta = \frac{R}{L}$$

The cutoff frequencies can be written in terms of  $\omega_0$  and  $\beta$  as follow:

$$\omega_1 = -\frac{\beta}{2} + \sqrt{\left(\frac{\beta}{2}\right)^2 + \omega_o^2}, \text{ and } \omega_2 = \frac{\beta}{2} + \sqrt{\left(\frac{\beta}{2}\right)^2 + \omega_o^2}$$

This shows that  $\omega_o$  is the geometric mean of  $\omega_1$  and  $\omega_2$ , i.e.,

$$\omega_o = \sqrt{\omega_1 \omega_2}$$

Notice that  $\beta$  is proportional to  $R$ , i.e., larger  $R$  results in a larger bandwidth. The resonant frequency ( $\omega_o = \frac{1}{\sqrt{LC}}$ ) is a function of  $L$  and  $C$ . Therefore, by adjusting  $L$  and

$C$  a desired resonant frequency is obtained, whereas by adjusting  $R$ , the bandwidth and the height of the response curve is adjusted. The sharpness of the resonance is measured quantitatively by the *quality factor*  $Q$ . This is defined as the ratio of the resonant frequency to the bandwidth.

$$Q = \frac{\omega_o}{\beta}$$


Substituting for  $\beta = \frac{R}{L}$  and  $\omega_o = \frac{1}{\sqrt{LC}}$  the quality factor can be expressed as

$$Q = \frac{\omega_o L}{R} = \frac{1}{\omega_o RC} = \frac{1}{R} \sqrt{\frac{L}{C}}$$

At resonance  $V_L$  and  $V_C$  are given by

$$V_L = j\omega_o LI(\omega_o) = jQV_i$$
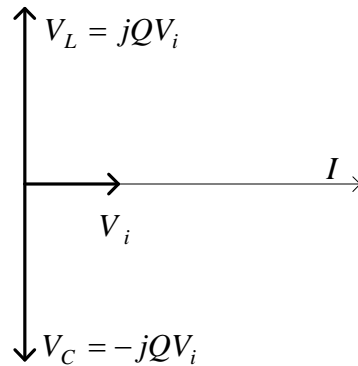
$$V_C = -j\frac{1}{\omega_o C} I(\omega_o) = -jQV_i$$




As it can be seen at resonance depending on the  $Q$  factor,  $V_L$  and  $V_C$  can be many times the supply voltage (voltage amplification).

For a circuit with a very high quality factor  $Q$ , the corner frequencies may be

approximated to  $\omega_1 = \omega_o - \frac{\beta}{2}$ , and  $\omega_2 = \omega_o + \frac{\beta}{2}$
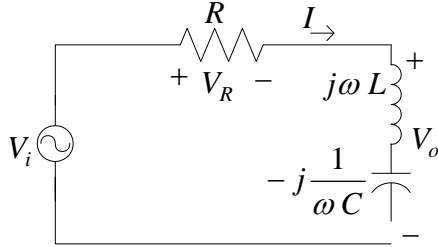
## Bandreject Filter

A bandreject filter is designed to stop all frequencies within a band of frequencies ( $\omega_1 < \omega < \omega_2$ ). In the series RLC circuit consider the output across the series combination  $L$  and  $C$ .




$$\frac{V_o}{V_i} = \frac{j(\omega L - \frac{1}{\omega C})}{R + j(\omega L - \frac{1}{\omega C})}$$

The voltage gain magnitude is

$$\frac{|V_o|}{|V_i|} = \frac{\omega L - \frac{1}{\omega C}}{\left[ R^2 + \left( \omega L - \frac{1}{\omega C} \right)^2 \right]^{1/2}}$$

At  $\omega = 0$ , the inductor behaves like a short circuit, and the capacitor behaves like an open circuit,  $I = 0$  and  $V_o = V_i$ , and the voltage gain is unity. At  $\omega = \infty$ , the inductor behaves like an open circuit and the capacitor behaves like a short circuit,  $I = 0$  and again  $V_o = V_i$ , and the voltage gain is unity. At resonance  $Z$  is purely resistive and

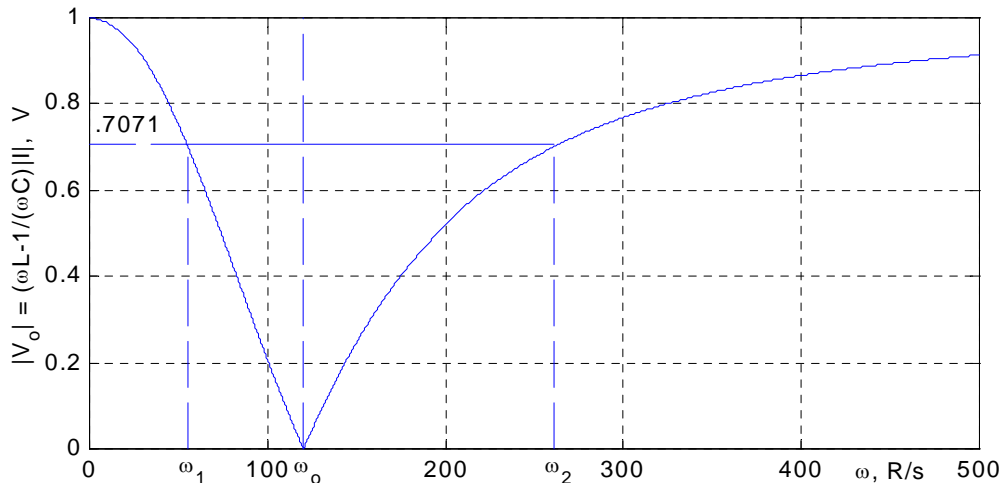$\omega L - \frac{1}{\omega C} = 0$ , thus  $\omega_o = \frac{1}{\sqrt{LC}}$ . Since the numerator of the voltage gain is zero, the gain drops to zero at  $\omega_o$ .



The cutoff frequencies, the bandwidth, and the quality factor are the same as the series RLC bandpass

filter,  $\beta = \frac{R}{L}$ ,  $\omega_1 = -\frac{\beta}{2} + \sqrt{\left(\frac{\beta}{2}\right)^2 + \omega_o^2}$ , and  $\omega_2 = \frac{\beta}{2} + \sqrt{\left(\frac{\beta}{2}\right)^2 + \omega_o^2}$