
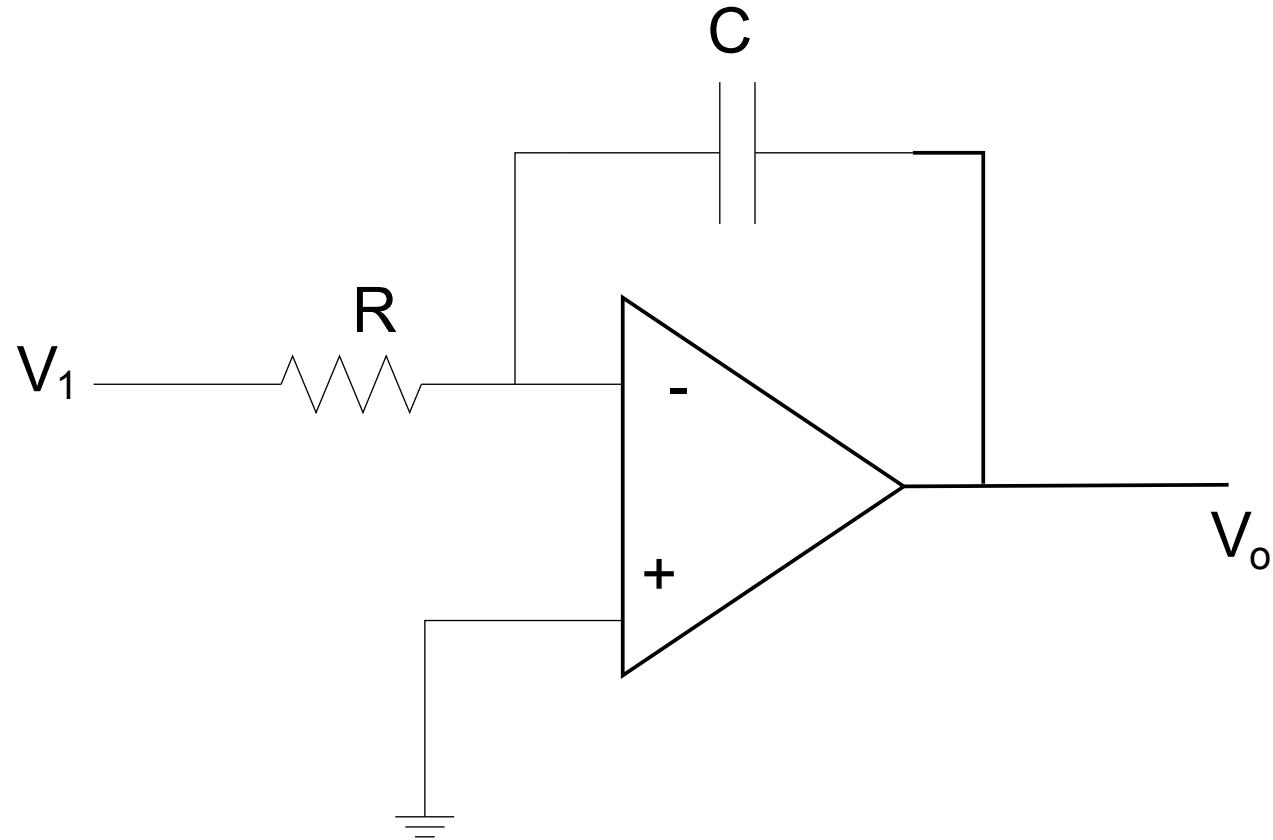


Practical OP-AMP Circuits

5. Integrator

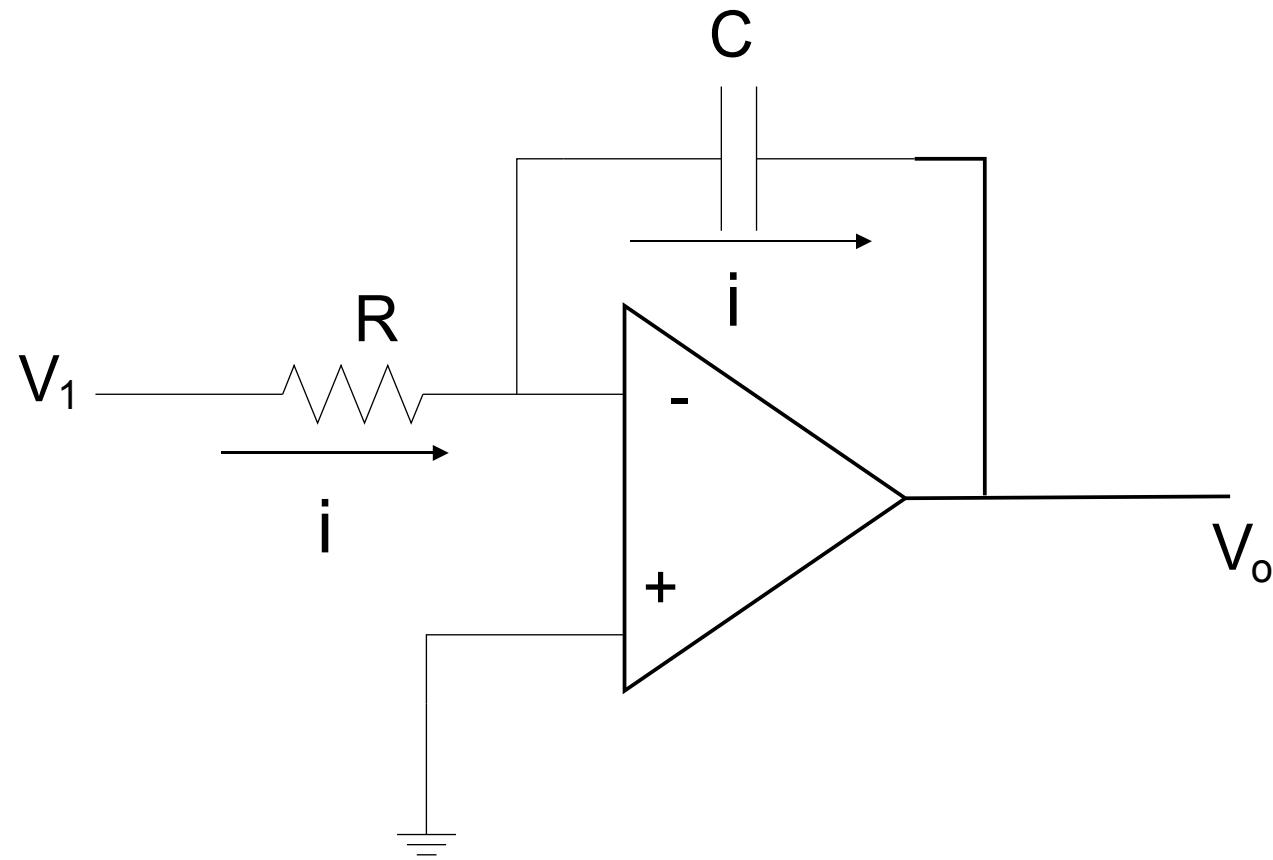



Integrator

$$v_1 - iR = 0$$


$$\text{or, } i = \frac{v_1}{R}$$


$$\text{Again, } 0 - \frac{1}{C} \int idt - v_o = 0$$

$$\text{or, } v_o = -\frac{1}{C} \int idt = -\frac{1}{C} \int \frac{v_1}{R} dt$$

$$\text{or, } v_o = -\frac{1}{RC} \int v_1 dt$$

6. Differentiator

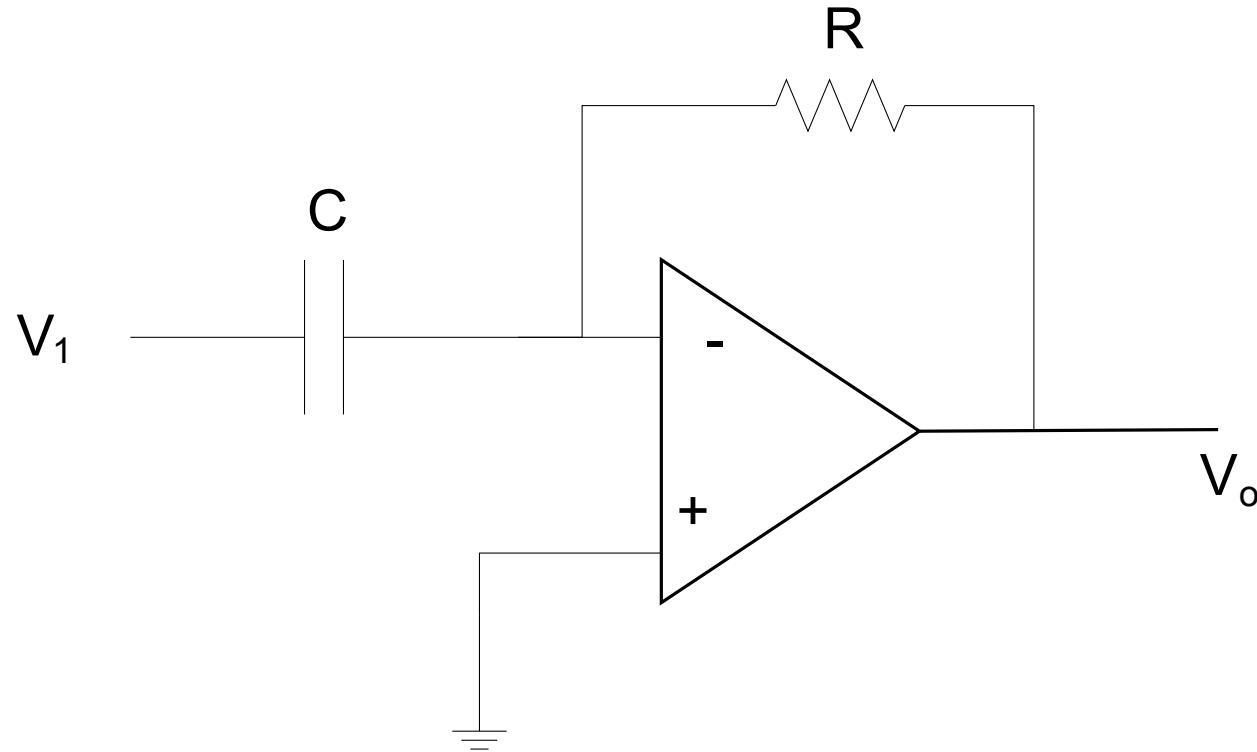

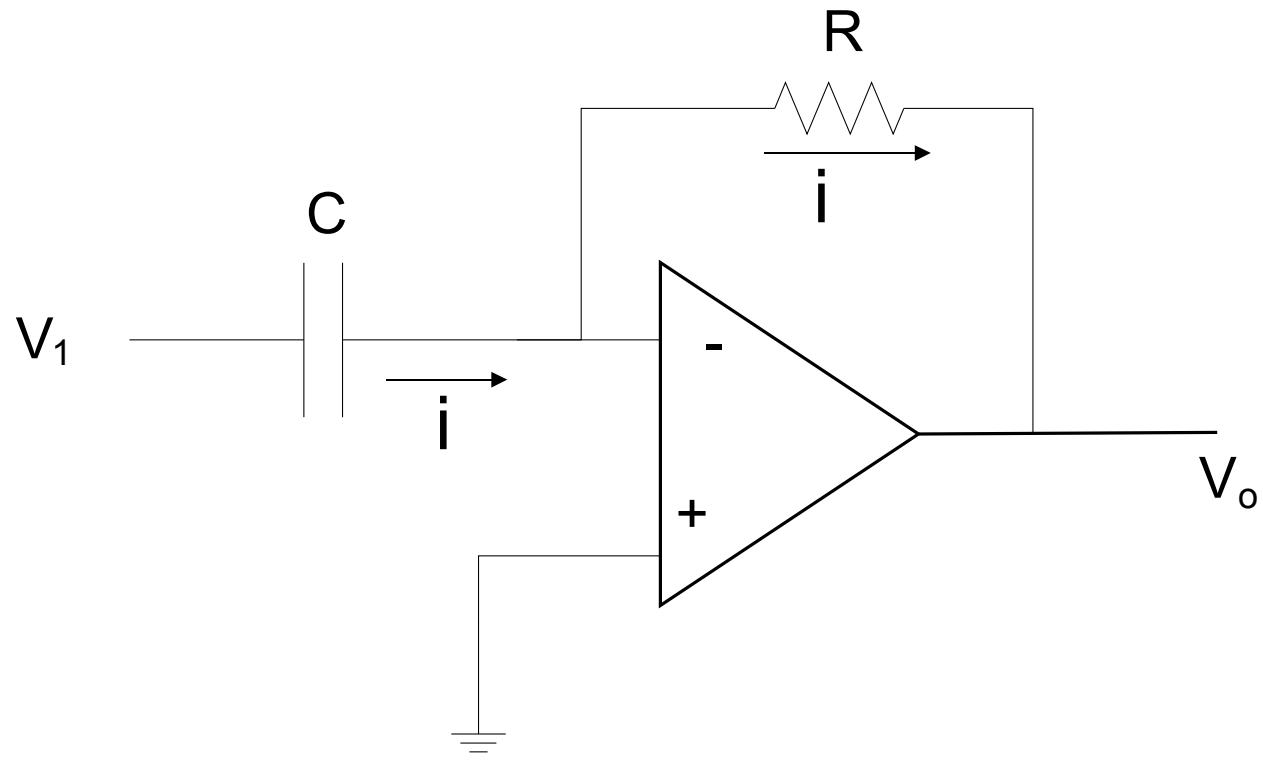

Differentiator

$$v_1 - \frac{1}{C} \int i dt = 0$$

or, $v_1 = \frac{1}{C} \int i dt$

or, $\frac{dv_1}{dt} = \frac{1}{C} i$


or, $i = C \frac{dv_1}{dt}$


Again, $0 - iR = v_o$

or, $v_o = -C \frac{dv_1}{dt} R$

or, $v_o = -RC \frac{dv_1}{dt}$

7. Voltage Subtractor or Difference

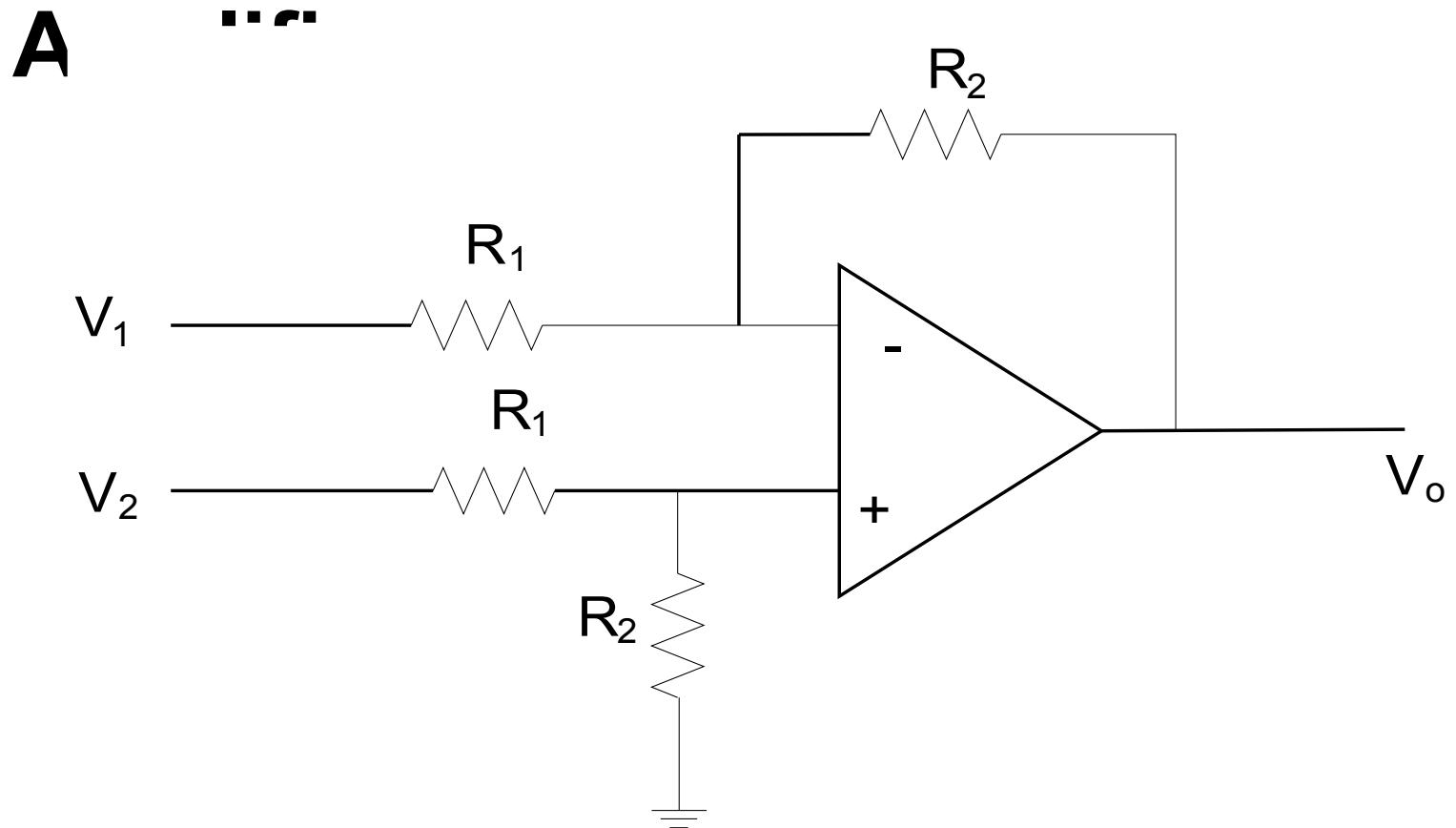

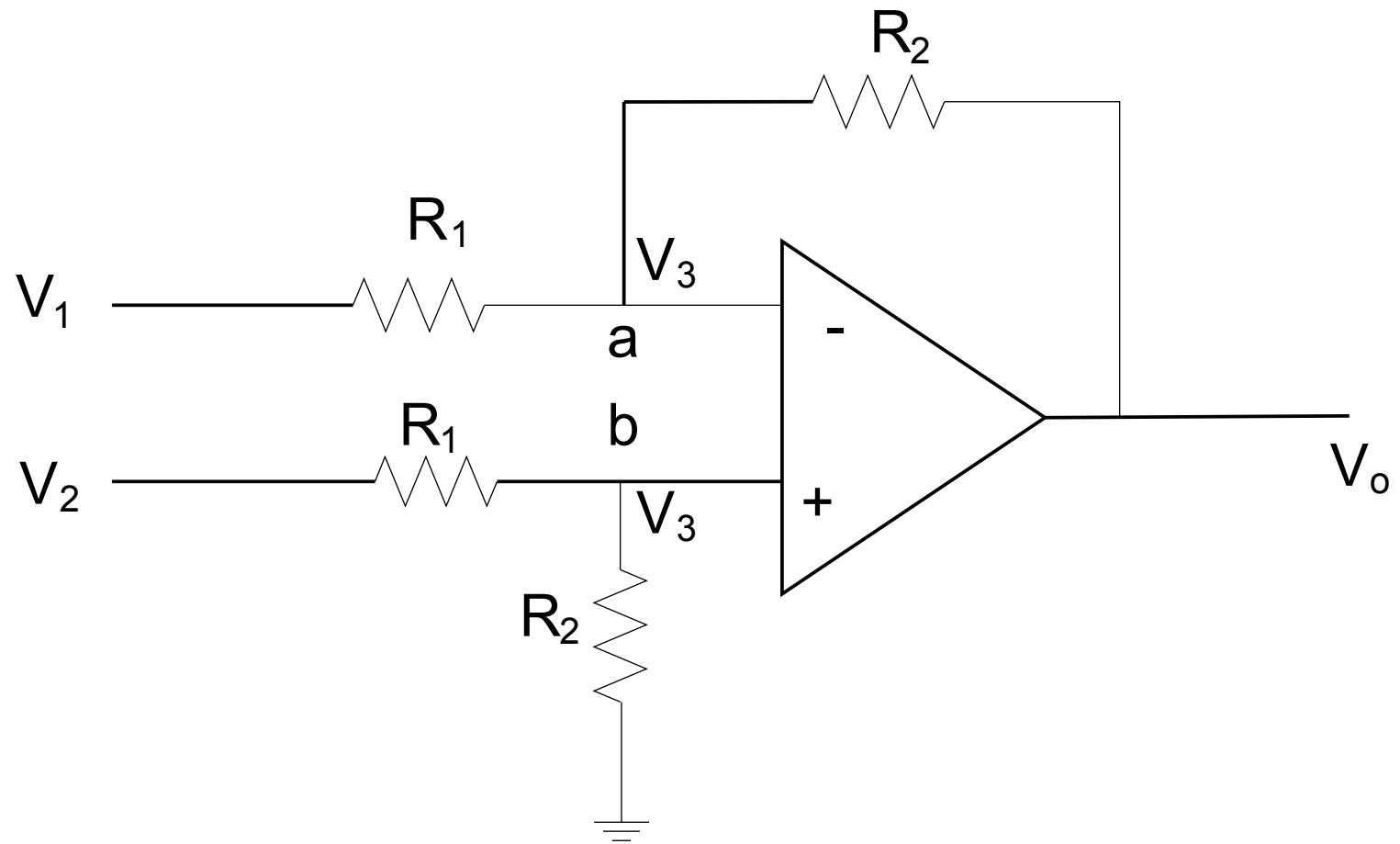

Applying KCL at node 'a' ,

$$(V_1 - V_3)/R_1 = (V_3 - V_0)/R_2 \quad (1)$$

Applying KCL at node 'b' ,

$$(V_2 - V_3)/R_1 = V_3/R_2 \quad (2)$$

Rearranging (1), we get,

$$(1/R_1 + 1/R_2)V_3 - V_1/R_1 = V_0/R_2 \quad (3)$$

Rearranging (2), we get,


$$(1/R_1 + 1/R_2)V_3 - V_2/R_1 = 0 \quad (4)$$

(3) – (4), we get,


$$(V_2 - V_1)/R_1 = V_o/R_2$$

or, $V_o = R_2/R_1(V_2 - V_1)$

Ex.1

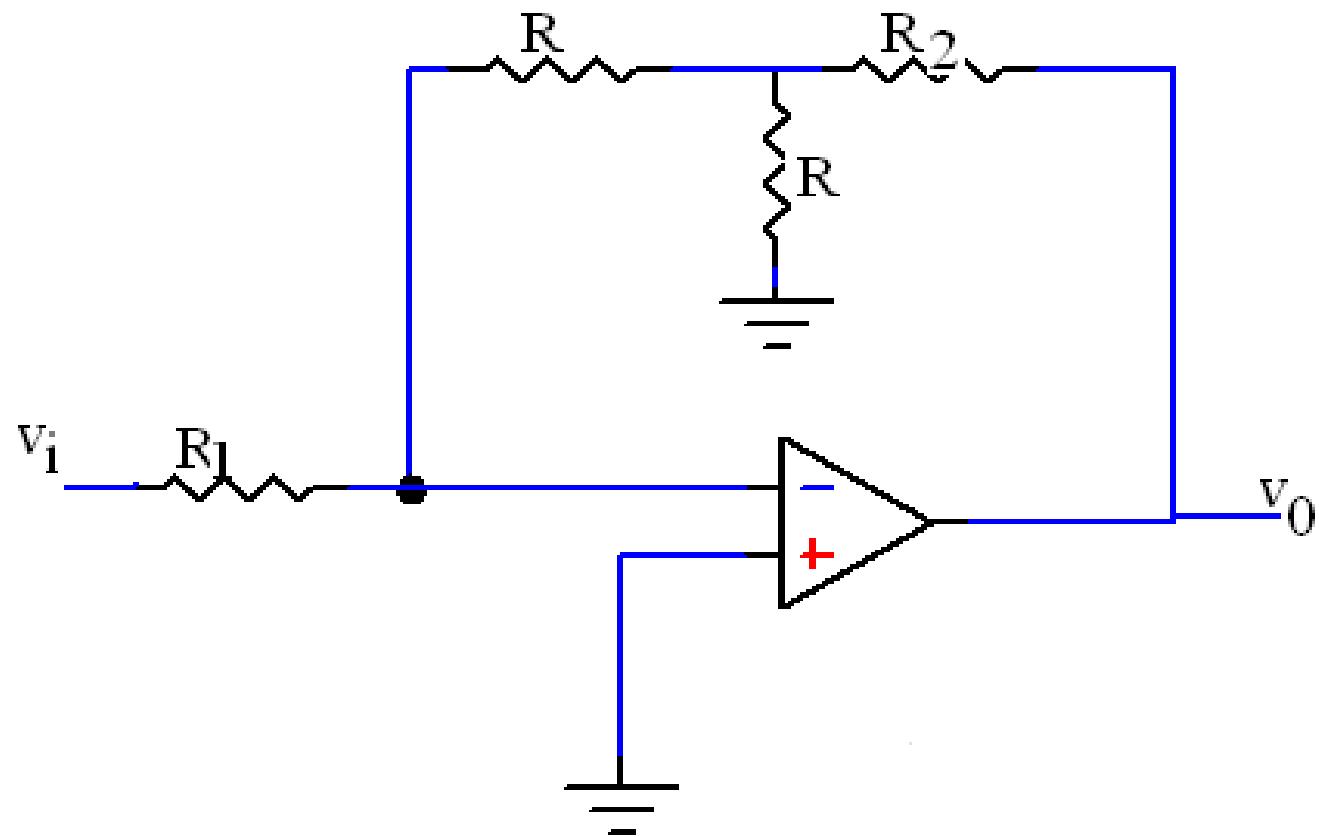

For the amplifier circuit find v_o/v_i

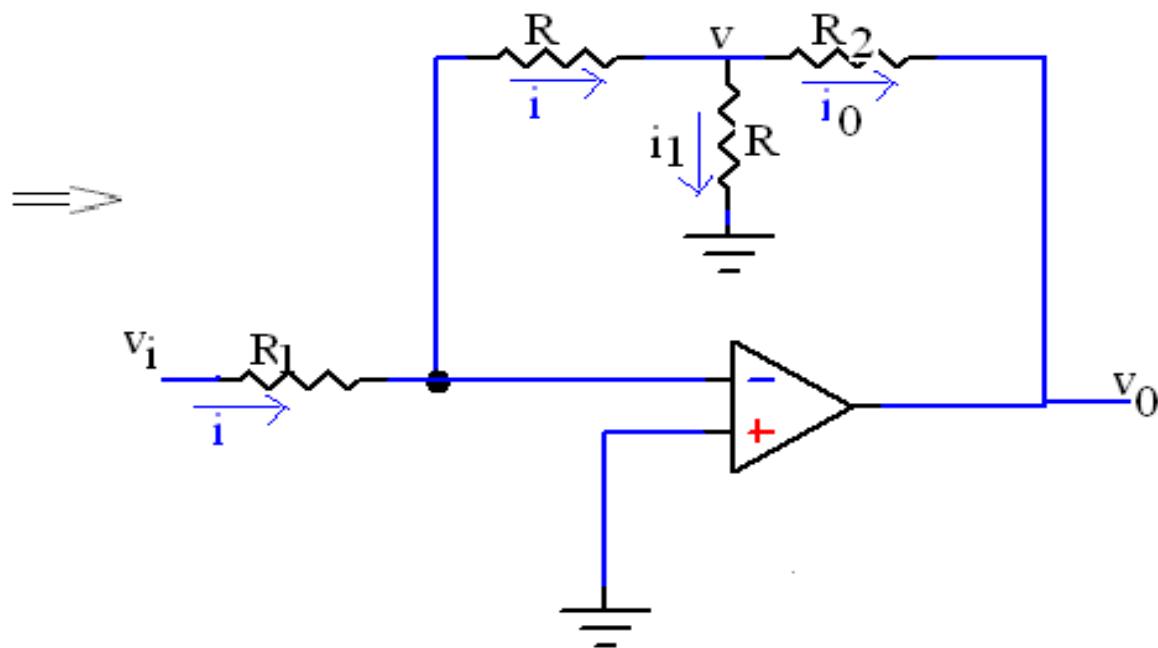

Solution :

$$\begin{aligned} i_o &= i - i_1 = v_i/R_1 - v/R = v_i/R_1 - (-iR)/R \\ &= v_i/R_1 + i = v_i/R_1 + v_i/R_1 = 2v_i/R_1 \end{aligned}$$


$$\begin{aligned} v_o &= v - i_o R_2 \\ &= -iR - 2v_i R_2 / R_1 \\ &= -v_i R / R_1 - 2v_i R_2 / R_1 \end{aligned}$$

or, $v_o = -v_i(R + 2R_2)/R_1$


Hence,

$$v_o/v_i = -(R + 2R_2)/R$$

Ex.1) Find V_o in the following circuit.

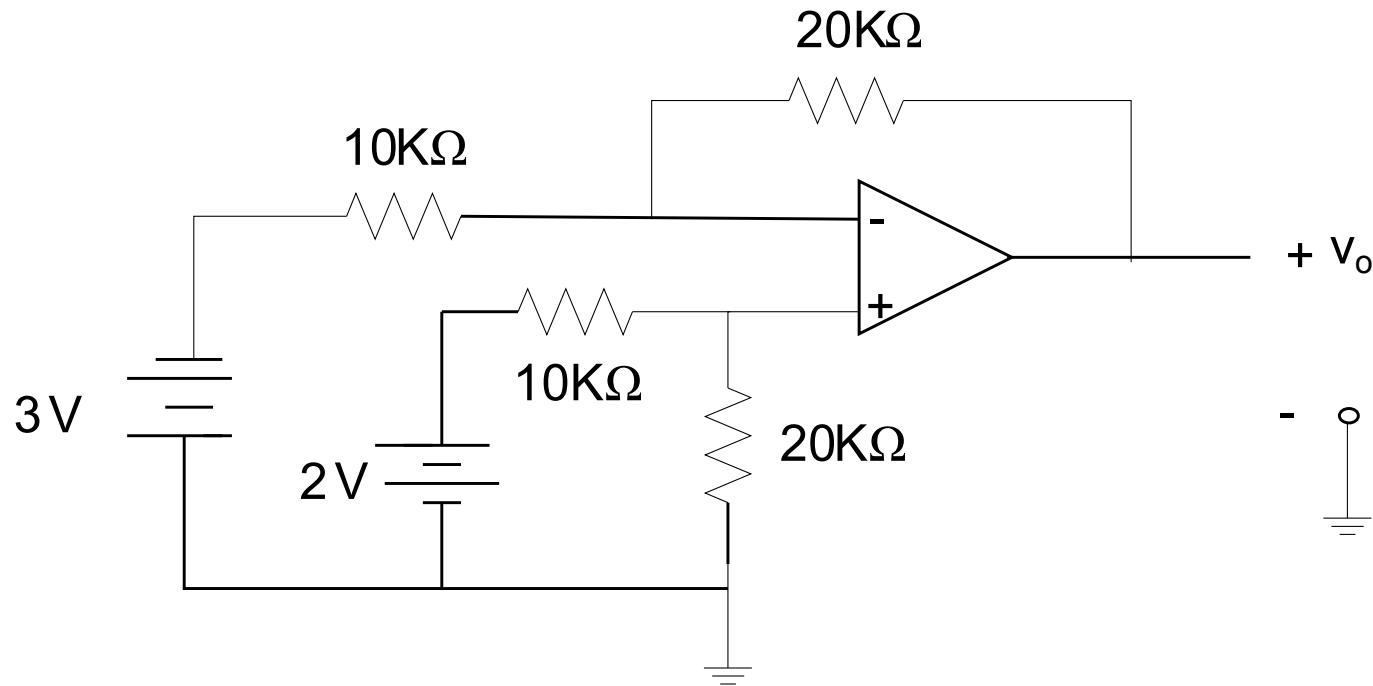

Solution

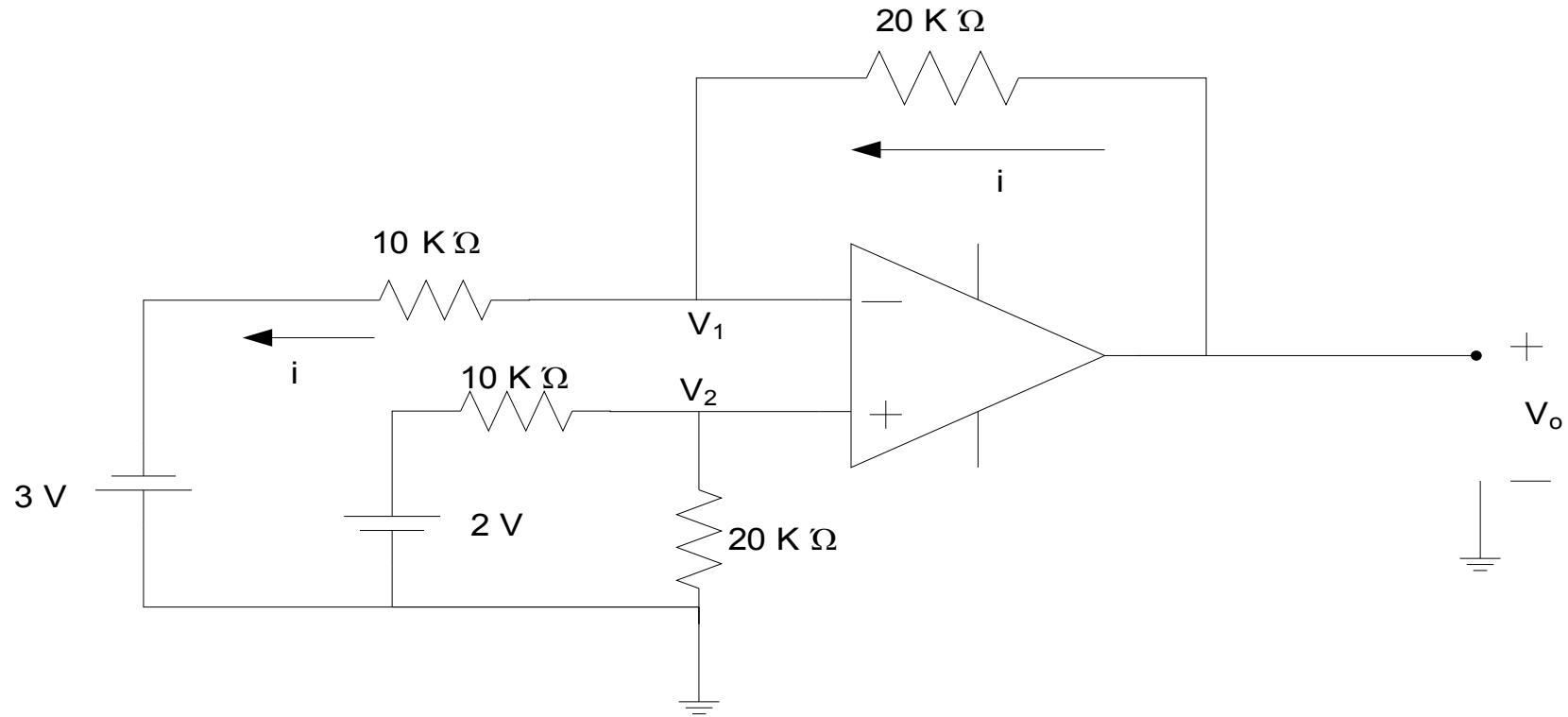

$$V_2 = 2V \times \frac{20}{20+10} = 2V \times \frac{20}{30} = \frac{4}{3}V$$

$$V_2 = V_1 = 4/3 V$$

$$\frac{V_o - V_1}{20} = \frac{V_1 + 3}{10}$$

$$\text{Or, } V_o - 4/3 = 2(4/3 + 3)$$

$$\text{Or, } V_o = 4/3 + 8/3 + 6 = 10 V$$